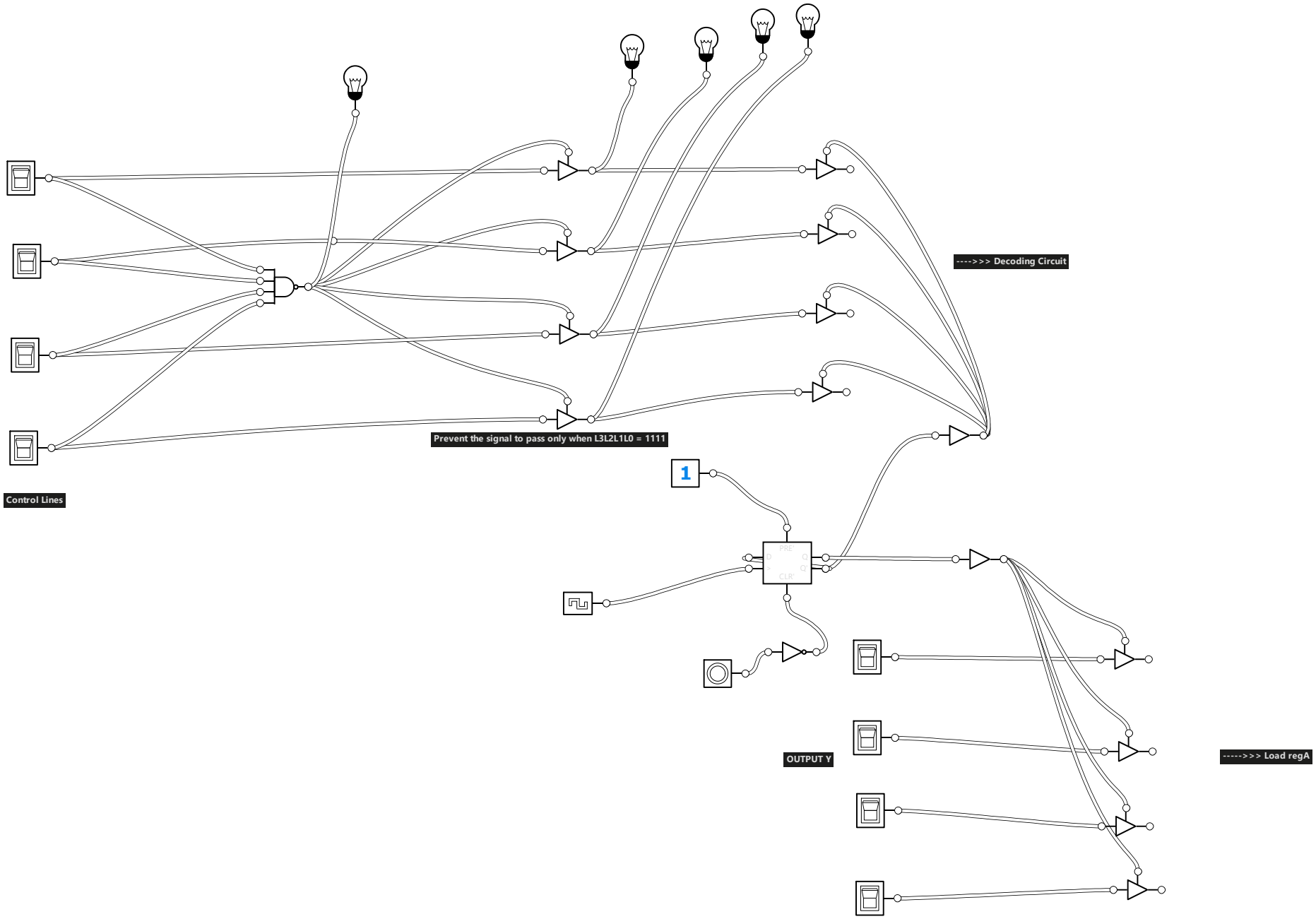
Control Lines
Prevent the signal to pass only when L3L2L1L0 = 1111
---->> Decoding Circuit
1
PRE
D
Q
CLR
OUTPUT Y
----->> Load regA