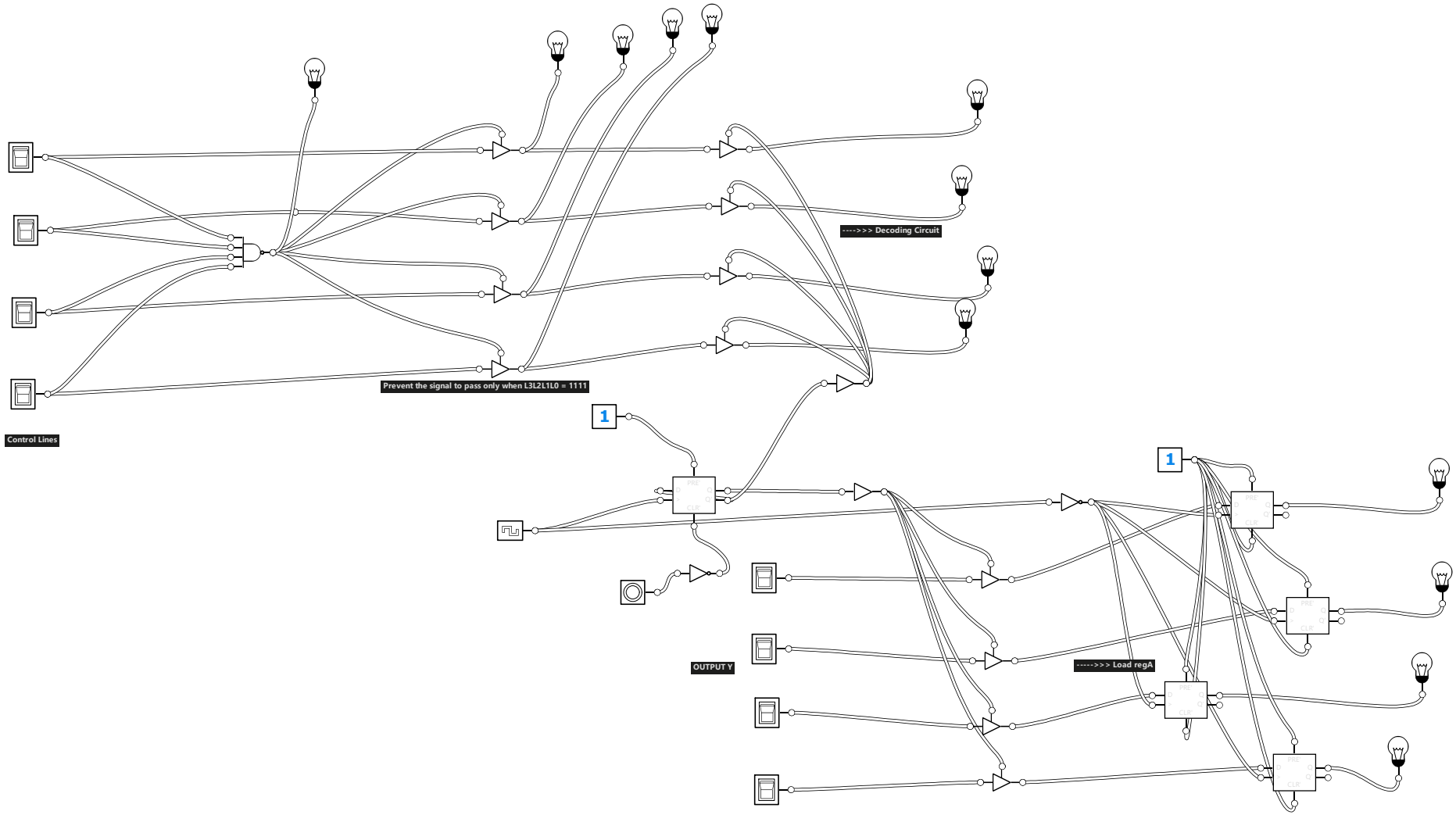
Control Lines
Prevent the signal to pass only when L3L2L1L0 = 1111
----->>> Decoding Circuit
1
OUTPUT Y
1
----->>> Load regA